

1.

**main program**

```

library ieee;
use ieee.std_logic_1164.all;
entity mux is
    port (a, b: in std_logic_vector(7 downto 0);
          sel: in std_logic_vector(1 downto 0);
          c: out std_logic_vector(7 downto 0));
end mux;
architecture example of mux is
begin
    process (a, b, sel)
    begin
        if (sel="00") then
            c <= "00000000";
        elsif (sel="01") then
            c <= a;
        elsif (sel="10") then
            c <= b;
        else
            c <= "ZZZZZZZZ";
        end if;
    end process;
end architecture;

```

Name	Value	Stimulator	. 20 . . 40 . . 60 . . 80 . .											
+ a		Binary Counter	00	05	0A	0F	14	19	1E	23	28			
+ b		Binary Counter	00	01	02	03	04	05	06	07	08			
- sel		Binary Counter	0	1		2		3		0				
a[sel(1)]														
a[sel(0)]														
+ c			00	0A		0F		04		05		22		00

2.

```


main program

entity circuit is
    port(a, b, c: in bit;
          y: out bit);
end circuit;

architecture myarch of circuit is
    signal x : bit;
begin
    x <= a and b;
    y <= x OR (not c);
end architecture;

```

 The signal A,B and C will have the respective frequencies of 12.5 MHz, 25MHz and 50 MHz. So the period for each signal is 80ns, 40ns and 20ns.



Bellow is the truth table from the assignment. Both the truth table and the waveforms match.

a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Grading criteria:

Q1 (50 points):

- Missing or incorrect code: -30
- Waveforms (pick one)
  - Missing or incorrect waveform: -20
  - Incomplete / unclear waveform: -5

Q2 (50 points):

- Code (pick one)
  - Missing or incorrect code: -30
  - Inefficient implementation (e.g. use of inout ports): -5
- Waveforms (pick one)
  - Missing or incorrect waveform: -20
  - Incomplete / unclear / done with other methods besides clocks: -10